



UNIVERSITY OF TEHRAN
Electrical and Computer Engineering Department
Digital Logic Design, ECE 367, Spring 1399-1400
Computer Assignment 5
State Machine Coding, Pre- and Post-Synthesis
Week 24

Name:

Date:

In this experiment, you are to design and implement a Moore and Mealy **10010** detector in SystemVerilog and implement and test them in Quartus. You will use pre-synthesis and post-synthesis descriptions of the same machine and compare simulation results. You will also use pre-synthesis descriptions of a Moore and a Mealy implementation and again see the differences.

- a. Write a complete behavioral SystemVerilog description of a Moore machine that detects the **10010** sequence. Use an asynchronous reset and the positive edge of the clock. This is your pre-synthesis design of the Moore **10010** detector.
 - i. Using a SystemVerilog testbench in the ModelSim simulation environment completely simulate your circuit. This is your pre-synthesis description.
 - ii. Import your Moore design in Quartus and build a symbol for it. Synthesize this design and see its timing, floor-plan and cells used. The synthesis process generates the post-synthesis description of your Moore 10010 detector. The .vo and .sdo files that are produced contain the netlist and timing of the synthesized circuit.
 - iii. Instantiate the pre- and post-synthesis descriptions of the Moore machine in a SystemVerilog testbench and compare the timing of the two descriptions.
- b. Write a complete behavioral SystemVerilog description of a Mealy machine that detects the **10010** sequence. Use an asynchronous reset and the positive edge of the clock. This is your pre-synthesis design of the Mealy **10010** detector.
 - i. Using a SystemVerilog testbench in the ModelSim simulation environment completely simulate your circuit. This is your pre-synthesis description.
 - ii. Import your Mealy design in Quartus and build a symbol for it. Synthesize this design and see its timing, floor-plan and cells used. The synthesis process generates the post-synthesis description of your Mealy **10010** detector. The .vo and .sdo files that are produced contain the netlist and timing of the synthesized circuit.
 - iii. Instantiate the pre- and post-synthesis descriptions of the Mealy machine in a SystemVerilog testbench and compare the timing of the two descriptions.
- c. In a SystemVerilog testbench instantiate the post-synthesis Moore and post-synthesis Mealy machines and run simulations to verify their operations and their differences. Make sure you apply data inputs that illustrate where the outputs are different.
 - i. In your testbench use an **assign** statement to show the differences between the two outputs. This can simple be done by XORing the two outputs.
 - ii. Be able to explain where the differences can and where they cannot be ignores.
 - iii. How can you adjust the XOR function to only show differences that are beyond just gate delay differences, and are due to changes on the inputs?