



University of Tehran
College of Engineering
School of Electrical and Computer Engineering



Digital Systems 1

Dr.Navabi

Homework 12

Soroush Mesforush Mashhad

SN:810198472

Tir 00

Question 1

Part A

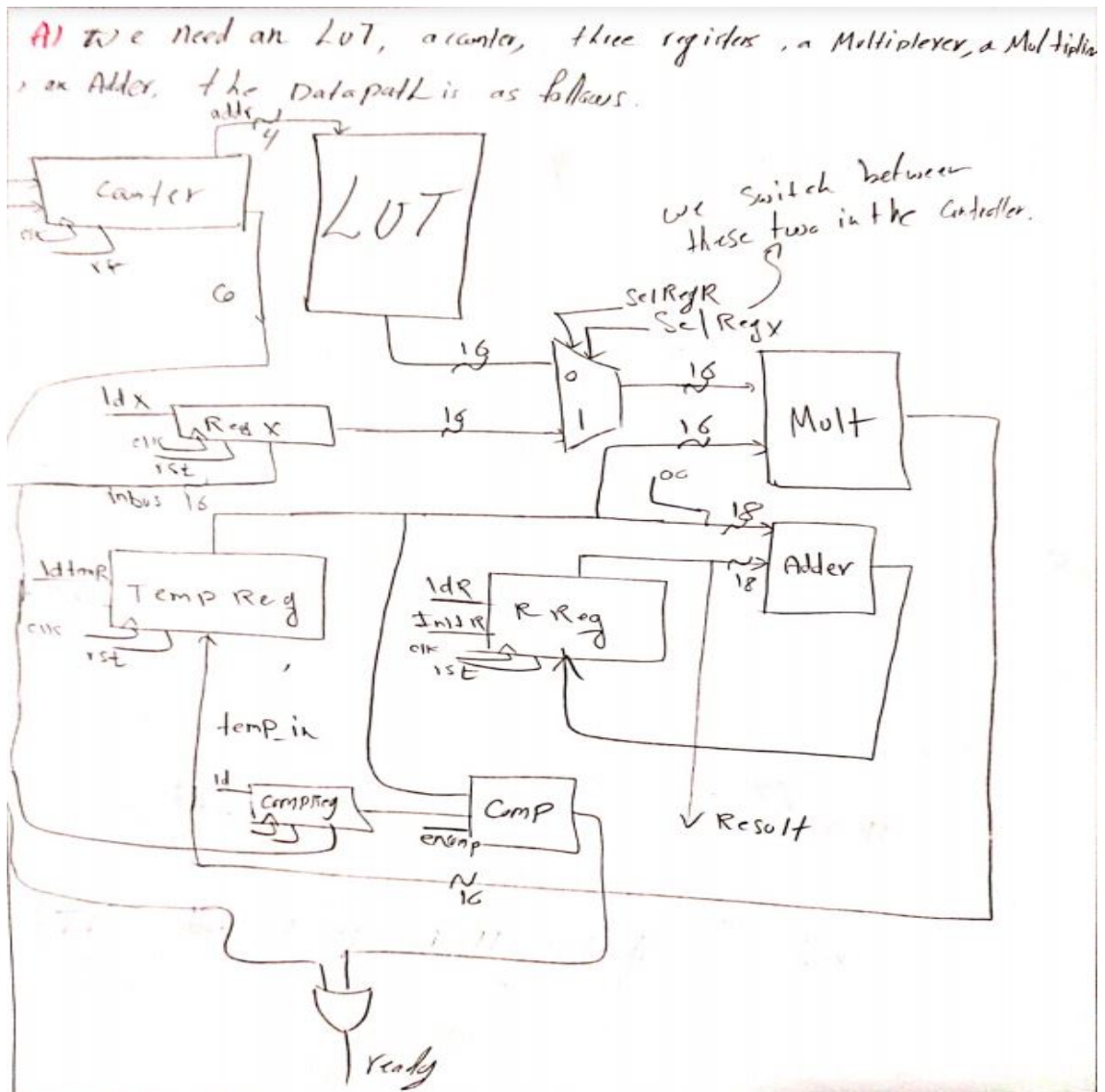


Figure 1: Datapath

Part B

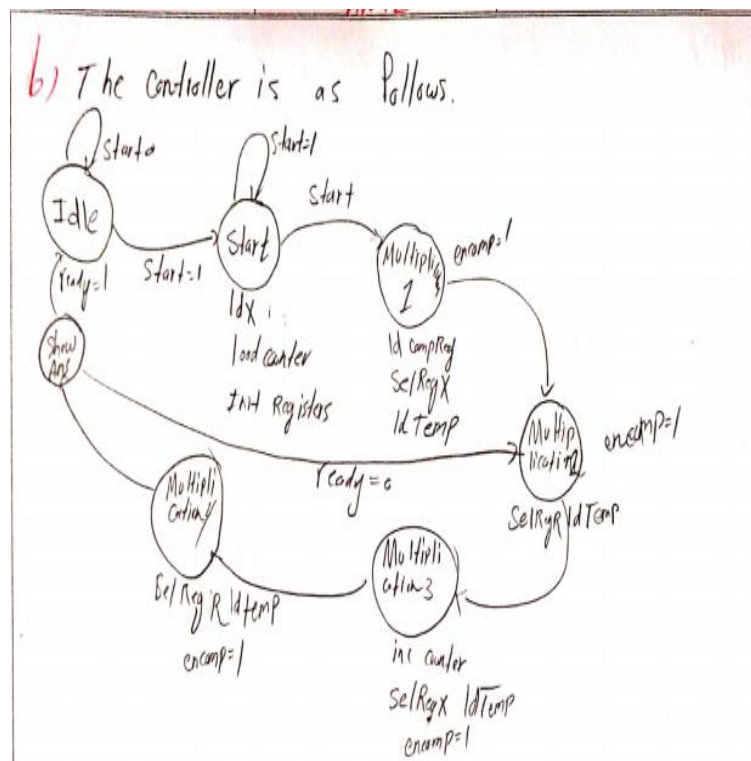


Figure 2: Datapath

Part C

The Verilog code for the controller is as follows.

```
`timescale 1ns/1ns
module Controller(input clk,rst,start,ready,output reg incCounter,loadCounter,ldX,ldR,ldTemp,ldCompReg,InitR,selRegx,selRegR,encomp);
    reg[2:0] ps,ns;
    parameter[2:0] Idle=0,Start=1,Multiplication1=2,Multiplication2=3,Multiplication3=4,Multiplication4=5,ShowAns=6;
    always@(posedge clk,posedge rst)begin
        if(rst) ps<=3'b000;
        else ps<=ns;
    end
    always@(ps,start,ready) begin
        case(ps)
            Idle:ns=start?Start:Idle;
            Start:ns=Multiplication1;
            Multiplication1:ns=Multiplication2;
            Multiplication2:ns=Multiplication3;
            Multiplication3:ns=Multiplication4;
            Multiplication4:ns=ShowAns;
            ShowAns:ns=ready?Idle:Multiplication1;
            default ns=Idle;
        endcase
    end
    always@(posedge clk,posedge rst)begin
        incCounter=0;loadCounter=0;ldX=0;ldR=0;ldTemp=0;InitR=0;selRegx=0;selRegR=0;encomp=0;
        case(ps)
            Idle:begin start<=1'b1;end
            Start:begin ldX<=1'b1;loadCounter<=1'b1;InitR<=1'b1;end
            Multiplication1:begin ldCompReg<=1'b1;selRegx<=1'b1;ldTemp<=1'b1;encomp<=1'b1;end
            Multiplication2:begin selRegR<=1'b1;ldTemp<=1'b1;encomp<=1'b1;end
            Multiplication3:begin selRegR<=1'b1;ldTemp<=1'b1;encomp<=1'b1;incCounter<=1'b1;end
            Multiplication4:begin selRegR<=1'b1;ldTemp<=1'b1;encomp<=1'b1;end
            ShowAns:ldR<=1'b1;
        endcase
    end
endmodule
```

Figure 3: Controller

Part D

d) the wiring is as follows.

 


Figure 4: Datapath