

1- a) we need a few registers, a Subtractor, two Counters and a Comparator. For the lower part of the circuit we subtract the Count data from $2^8 = 256$ and load it into another Counter. then we get the readmem from it into the memory. and so on.
we can also add a register here

