




Digital Systems 1 CA1 Report

Soroush Mesforush Mashhad(810198472)

Project Generated Files:

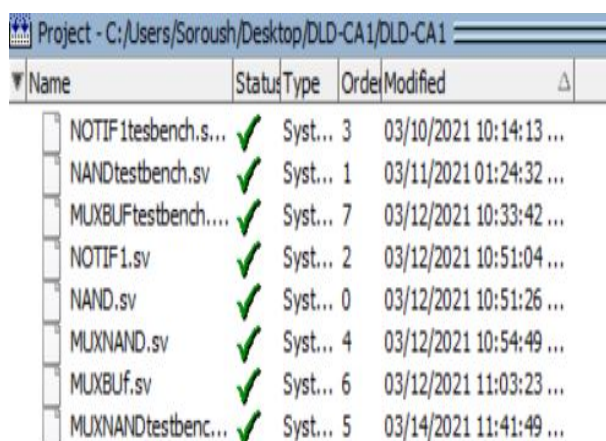A view of all my generated and compiled files can be seen in the following attachment:



Name	Status	Type	Order	Modified
NOTIF1testbench.s...	✓	Syst...	3	03/10/2021 10:14:13 ...
NANDtestbench.sv	✓	Syst...	1	03/11/2021 01:24:32 ...
MUXBUFtestbench....	✓	Syst...	7	03/12/2021 10:33:42 ...
NOTIF1.sv	✓	Syst...	2	03/12/2021 10:51:04 ...
NAND.sv	✓	Syst...	0	03/12/2021 10:51:26 ...
MUXNAND.sv	✓	Syst...	4	03/12/2021 10:54:49 ...
MUXBUF.sv	✓	Syst...	6	03/12/2021 11:03:23 ...
MUXNANDtestbenc...	✓	Syst...	5	03/14/2021 11:41:49 ...

Figure 1: Generated and Compiled .sv files

Question 1:

- Hand Simulation:

 


Figure 2: Hand Simulation

- Verilog Code & Testbench:

```

1 //In this module I have created a NAND gate
2 `timescale 1ns/1ns
3 module NAND (input i1,i2,output out);
4 //Here I have defined the needed wires and
5 wire y;
6 supply1 Vdd;
7 supply0 Gnd;
8 //Here we connect the pmos and nmos transistors
9 pmos # (5,6,7) T1(out,Vdd,i1);
10 pmos # (5,6,7) T2(out,Vdd,i2);
11 nmos # (3,4,5) T3(y,Gnd,i2);
12 nmos # (3,4,5) T4(out,y,i1);
13 endmodule
14
15 `timescale 1ns/1ns
16 module NANDtestbench();
17 logic aa=0;
18 logic bb=0;
19 wire ww;
20 NAND uut(aa,bb,ww);
21 initial begin
22     #30 aa=1;
23     #30 bb=1;
24     #30 aa=0;bb=0;
25     #30 aa=1;bb=1;
26     #30 bb=0;
27     #40 $stop;
28 end
29 endmodule

```

Figure 3: Verilog Code & Testbench

- Waveform:


 


Figure 4: NAND Waveform

Question 2:

- Hand Simulation:

Tri-State Buffer		
a	EN	w
1	1	0
1	0	Z
0	1	1
0	0	Z

 

Worst case to 1: This happens when we transition from (0,0) \rightarrow (0,1) in which case we shall have a 12ns delay

Worst case to 0: This happens when we transition from (0,1) \rightarrow (1,1) in which case we have 14ns to send 0 from the pmos, so the delay is 14ns

Worst case to Z: This happens when we transition from (0,1) \rightarrow (0,0) in which case we shall have a 12ns delay.

Figure 5: Hand Simulation

- Verilog Code & Testbench:

```
//In this module I have created a tri-state buffer
`timescale 1ns/1ns
module NOTIF1(input a,En,output w);
//Here I have defined the needed wires and supplies
    wire x,y,z;
    supply1 Vdd;
    supply0 Gnd;
//Here we connect the pmos and nmos transistors accordingly.
    pmos # (5,6,7) T1(x,Vdd,En);
    nmos # (3,4,5) T2(x,Gnd,En);
    pmos # (5,6,7) T3(y,Vdd,a);
    pmos # (5,6,7) T4(w,y,x);
    nmos # (3,4,5) T5(w,z,En);
    nmos # (3,4,5) T6(z,Gnd,a);
endmodule

`timescale 1ns/1ns
module NOTIF1testbench();
    logic aa=1;
    logic EN=1;
    wire ww;
    NOTIF1 UUT(aa,EN,ww);
    initial begin
        #30 aa=0;
        #30 EN=0;
        #30 EN=1;
        #30 aa=1;
        #50 $stop;
    end
endmodule
```

Figure 6: Tri-State Buffer Code & Testbench

- Waveform:

 


Figure 7: Tri-State Buffer Waveform

Question 3:

- Hand Simulation:

4 to 1 MUX with 2 input NAND gates only:



In the following design only two input NAND gates designed in problem 1 have been used.

Figure 8: Hand Simulation

First we should note that the worst case delays to 1 and 0 for a NOT gate made with a NAND gate shall be 5ns and 8ns respectively, therefore we can have odd numbers during the simulation, whilst simulating I encountered a 41 ns delay when transitioning to 1 and also 0 and a weird 44ns delay which shall be depicted in the future parts.

- Verilog Code & Testbench:

```
//In this Module I've created a 4 to 1
//MUX with 2 input NAND gates only.
`timescale 1ns/1ns
module MUXNAND(input a,b,c,d,s0,s1, output out);
//Here I have defined the needed wires.
    wire x,y,z,w,f,h,k,l,m,o;
/*Based on the design for a 4 to 1 MUX
with 2 input NAND gates,I've used the
NAND gate from problem 1 (11 gates) and connected
them in the proper manner.*/
    NAND T1 (.i1(s0),.i2(s0),.out(x));
    NAND T2 (.i1(s0),.i2(d),.out(o));
    NAND T3 (.i1(s1),.i2(k),.out(m));
    NAND T4 (.i1(s1),.i2(s1),.out(y));
    NAND T5 (.i1(b),.i2(x),.out(z));
    NAND T6 (.i1(o),.i2(z),.out(k));
    NAND T7 (.i1(s0),.i2(c),.out(w));
    NAND T8 (.i1(x),.i2(a),.out(f));
    NAND T9 (.i1(w),.i2(f),.out(h));
    NAND T10 (.i1(h),.i2(y),.out(l));
    NAND T11 (.i1(l),.i2(m),.out(out));
endmodule

`timescale 1ns/1ns
module MUXNANDtestbench();
    logic aa,bb,cc,dd,ss0,ss1;
    wire oout;
    integer i=0;
    MUXNAND UUT(aa,bb,cc,dd,ss0,ss1,oout);
    initial begin
        while(i<64) begin
            #100;
            {aa,bb,cc,dd,ss0,ss1}=64-i;
            #100;
            {aa,bb,cc,dd,ss0,ss1}=i;
            i=i+1;
        end
        #100 $stop;
    end
endmodule
```

Figure 9: 4to1 MUX(With NAND) Code & Testbench

- Waveform:

 


Figure 10: 4to1 MUX(With NAND) Waveform

Question 4:

- Hand Simulation:

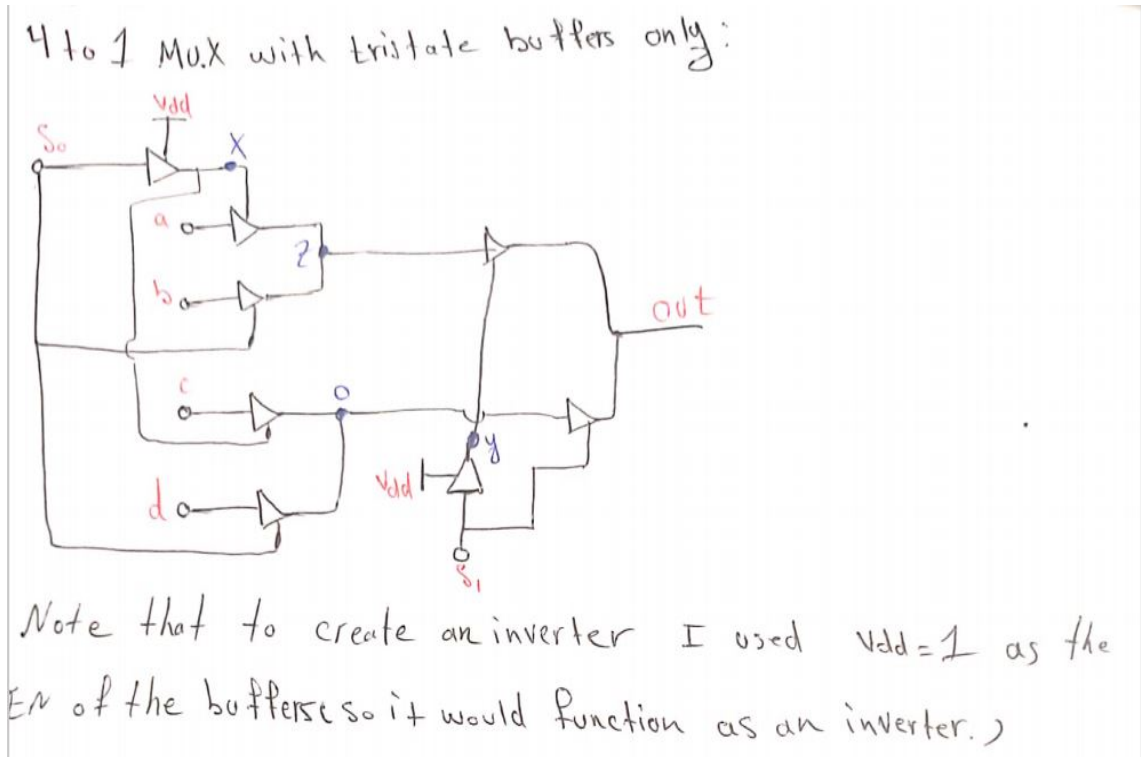


Figure 11: Hand Simulation

In this design I have only used Tri-State buffers (even to implement the not gate), whilst simulating I encountered a 36ns delay for transitioning to 1 and 0 respectively.

- Verilog Code:

```

/*In this module I've created a 4 to 1
MUX using a Tristate buffer only.*/
`timescale 1ns/1ns
module MUXBUF(input a2,b2,c2,d2,s02,s12,output out2);
//Here I've defined the needed wires.
    wire x,y,z,o;
/*The supply is used to connect
to the En of the buffers to create an inverter*/
    supply1 Vdd;
/*Based on the design for a 4 to 1 MUX
with tri-state buffers,I've used the
Buffer from problem 2 (8 gates) and connected
them in the proper manner.*/
    NOTIF1 G1 (.a(s02),.En(Vdd),.w(x));
    NOTIF1 G2 (.a(a2),.En(x),.w(z));
    NOTIF1 G3 (.a(c2),.En(s02),.w(z));
    NOTIF1 G4 (.a(b2),.En(x),.w(o));
    NOTIF1 G5 (.a(d2),.En(s02),.w(o));
    NOTIF1 G6 (.a(s12),.En(Vdd),.w(y));
    NOTIF1 G7 (.a(o),.En(s12),.w(out2));
    NOTIF1 G8 (.a(z),.En(y),.w(out2));
endmodule

```

```

`timescale 1ns/1ns
module MUXBUFTestbench();
    logic aa,bb,cc,dd,ss0,ss1;
    wire oout;
    integer i=0;
    MUXBUF UUT(aa,bb,cc,dd,ss0,ss1,oout);
    initial begin
        while(i<64) begin
            #100;
            {aa,bb,cc,dd,ss0,ss1}=64-i;
            #100;
            {aa,bb,cc,dd,ss0,ss1}=i;
            i=i+1;
        end
        #100 $stop;
    end
endmodule

```

Figure 12: 4to1 MUX(With Tri-State Buffer) Code and Testbench

- Waveform:

 


Figure 13: 4to1 MUX(With Tri-State Buffer) Waveform

Question 5:

The delays are less for the MUX made with Tri-state buffers compared to the one made with NAND gates, this is because of the structural layout of transistors in the said designs. The design for problem 3 has 11 NAND gates which consists of 44 PMOS and NMOS transistors and the design for problem 4 has 8 Tri-State buffers which is made up of 48 PMOS and NMOS transistors therefore I think it has a greater power consumption.